

First Semester B.C.A. Degree Examination
October / November 2018
(2016-17 Syllabus)

BCA 440 : DIGITAL COMPUTER FUNDAMENTALS

Time : 3 Hours

Max. Marks : 80

I. Answer ALL the following.**5x1=5**

1. Perform 2's complement on 1101011.
2. $A + \bar{A}B = \underline{\hspace{2cm}}$.
3. Define minterm.
4. Define de-multiplexer.
5. What is the drawback of SR - FF.

II. Answer any FIVE of the following:**15x5=75**

6. a) Convert the following:
 - i) $147.71 = ?_{(2)}$
 - ii) $304.3024_{(8)} = ?_{(16)}$
 - iii) $BCA_{(16)} = ?_{(8)}$
 b) Solve using 1's and 2's complement of subtraction.
 - i) $78 - 62$ ii) $62 - 78$
 c) i) How do you convert binary to gray and vice-versa. Give example for each.
 ii) Expand BCD. **(5+5+5)**
7. a) Explain all the basic gates with circuit and truth table.
 b) State and prove Demorgan's theorem.
 c) Simplify the following using boolean laws
 - i. $Y = (A + B) (\bar{A} \bar{C} + C) (\bar{B} + A C)$
 - ii. Show that $\bar{A} \bar{B} C + \bar{B} C \bar{D} + \bar{A} \bar{D} = \overline{ABCD}$ **(5+5+5)**
8. a) Convert $AB + \bar{B}\bar{C}$ to its standard form and show SOP and POS are complement to each other.
 b) i. Write the outlet of 3 and 4 variable K-map.
 ii. List out the rules to simplify boolean expression using K-map.
 c) Simplify $Y = \bar{A} \bar{B} \bar{C} + \bar{B} C \bar{D} + \bar{A} B C \bar{D} + A \bar{B} \bar{C}$ using K-map and realise the simplified Expression using NAND gates only. **(5+5+5)**

9. a) Simplify
 $F(A, B, C, D) = \pi_m(0, 5, 7) \cdot d(1, 4, 8)$
using K-map and realise the simplified expression using NOR gates only.
- b) Solve by using QM - method to find the prime implicants of
 $F(w, x, y, z) = \sum_m(0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$
- c) For the above QM - method problem find essential prime Implicants and realise the result with basic gates. **(5+5+5)**
10. a) Design a full adder using two half adders.
- b) What is a multiplexer ? Explain the working of 4:1 multiplexer.
- c) Design and explain two bit magnitude comparator. **(5+5+5)**
11. a) What is a flip flop ? Explain the working of JK - FF.
- b) Explain: i. T - FF ii. D - FF
- c) What is a shift register ? Explain SISO and PISO shift registers. **(5+5+5)**
12. a) Design and explain the working of 4-bit ripple up counter.
- b) Explain 3-bit updown counter.
- c) Explain the working of mod-11 counter. **(5+5+5)**

* * * * *